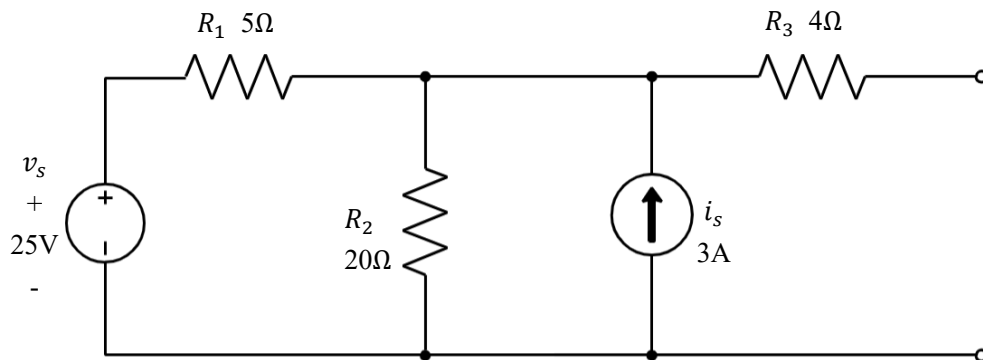





**II.** Find the Thévenin and Norton equivalent circuit of the following circuit and calculate the maximal output power  $P_{\max}$  of the terminal.

10




**III.** The following circuit is operating in steady state with the switch close prior to  $t = 0$ . Find the expression for  $v_C(t)$  when  $t < 0$  and  $t \geq 0$ . Calculate the voltage  $i_L(t)$  when  $t = 2s$ .

10

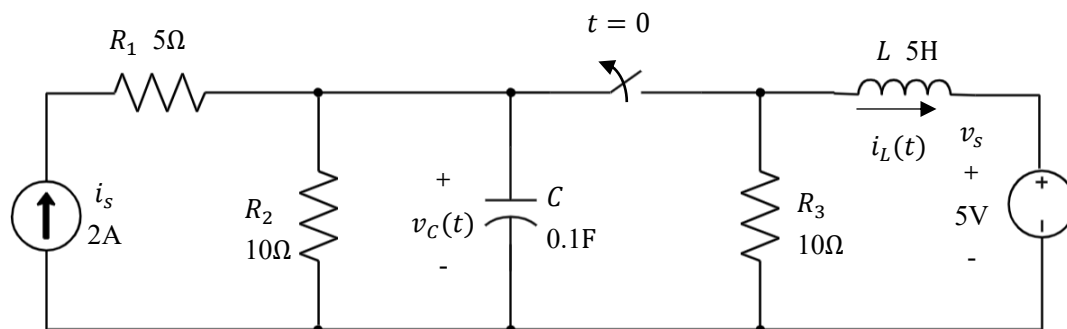


**IV.** Consider the circuit shown in the following figure. Find the maximal power output  $P_{\max}$ .

10

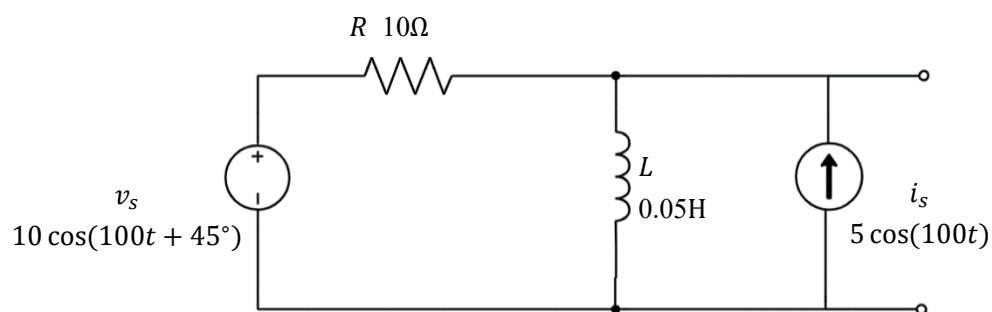

V. Consider the emitter-follower amplifier shown in the following figure.

**Total**  
**20**

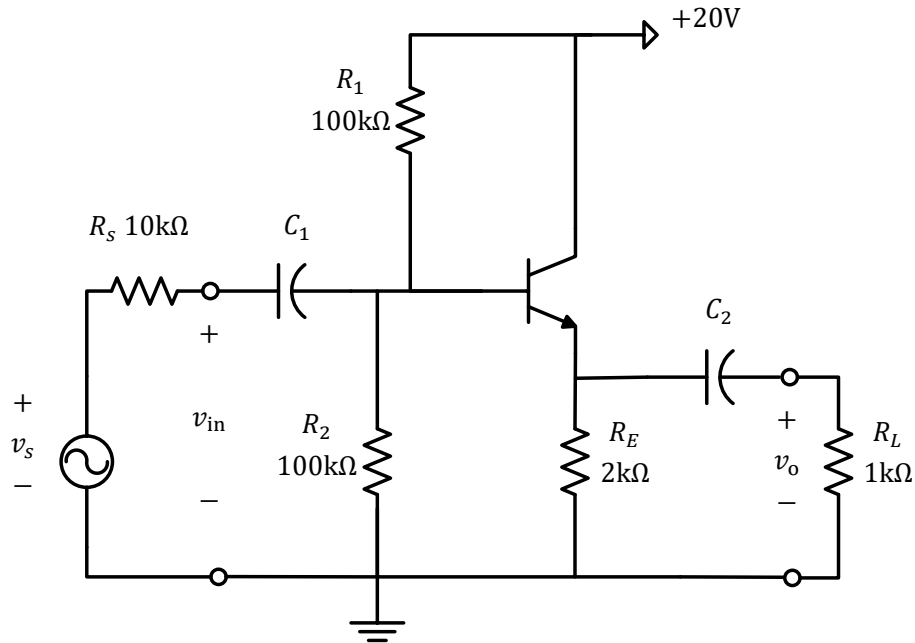

The BJT transistor has  $\beta = 100$  and  $V_{BEQ} = 0.7V$ .

**a)** Draw the bias circuit to determine the Q point and calculate the values of  $I_{CQ}$ , find the value of  $r_{\pi}$ .


**10**

**b)** Draw the small signal equivalent circuit and calculate the voltage gain  $A_v$ , input impedance  $Z_{in}$ , output impedance  $Z_o$ , and power gain  $G$ , assuming that the coupling capacitors are short circuits for the ac signal.

**10**

**VI.** Consider the common-source amplifier shown in the following figure.

**Total**  
**20**

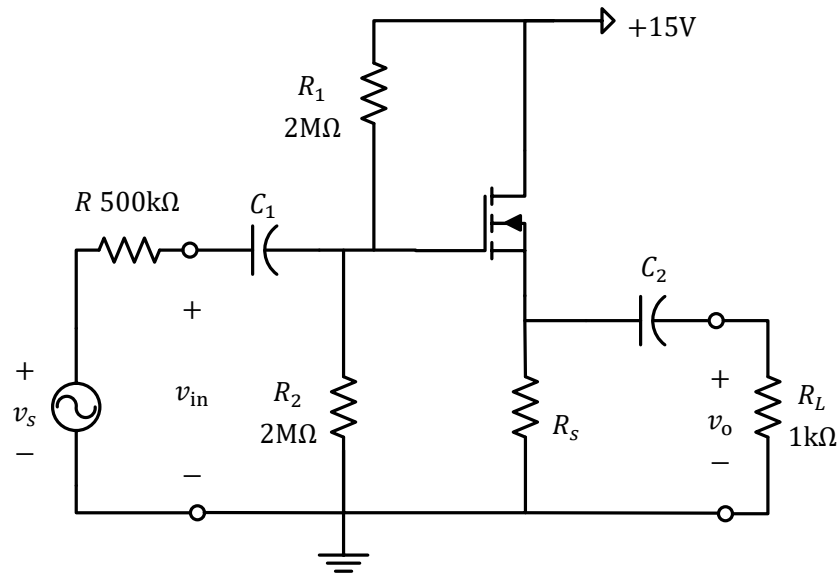

The NMOS transistor in the above figure has  $KP = 50\mu\text{A}/\text{V}^2$ ,  $L = 2\mu\text{m}$ ,  $W = 160\mu\text{m}$ ,  $V_{to} = 1\text{V}$ , and  $r_d = \infty$ .

**a)** Find the value required for  $R_S$  to achieve  $I_{DQ} = 10\text{mA}$ .

**10**

**b)** Draw the small signal equivalent circuit and compute the voltage gain  $A_v$ , input impedance  $Z_{in}$ , and power gain  $G$ , assuming that the coupling capacitors are short circuits for the ac signal.

**10**

**VII.** Design a PID controller using Op-amp based on the following equation:

**10**

$$v_o = 5v_{in}(t) - 4 \int_0^t v_{in}(t)dt - 10 \frac{dv_{in}(t)}{dt}$$

**VIII.** Construct a Karnaugh map for the logic function:

$$F = \bar{A}\bar{B}\bar{C}D + \bar{A}\bar{B}CD + A\bar{B}\bar{C}D + A\bar{B}CD + \bar{A}BC\bar{D} + ABC\bar{D}$$

Find the minimal sum of product expression, and implement the logic circuit.

**10**

Name \_\_\_\_\_ Student ID           School \_\_\_\_\_ Major/Class \_\_\_\_\_ Seat No. \_\_\_\_\_

(DO NOT WRITE YOUR ANSWER IN THIS AREA)

[illegible]

**WARNING: MISBEHAVIOR AT EXAM TIME WILL LEAD TO SERIOUS CONSEQUENCE.**

# SCUT Final Exam

[illegible]

## I.

## II.

### III.

**IV.**

**V.**

**VI.**

**VII.**

**VIII.**